

Semiconductor 2

PH-122




PN JUNCTION

- If a piece of silicon is partially doped with p type and partially with n type semiconductor, pn junction formed
- P region has large number of holes than n type and n region has large number of electrons than p type.

Formation of depletion region:

- Free electrons near the junction begin to diffuse across the junction into p type and combine with holes and create a layer of -ve charges (ions) near junction
- When electrons diffuse across the junction ,creates a layer of +ve charges(ions) near the junction
- At one point , the migratory action is stopped because an additional electrons from the N region are repelled by the net negative charge of the p region. Similarly, an additional holes from the P region are repelled by the net positive charge of the n region. Net result a creation of a thin layer of each side of the junction which is depleted (emptied) of mobile charge carrier. This is known as DEPLETION LAYER.
- Depletion region acts as a barrier to the further movement of electrons across the junction
- Thickness is of the order of 10-6meter

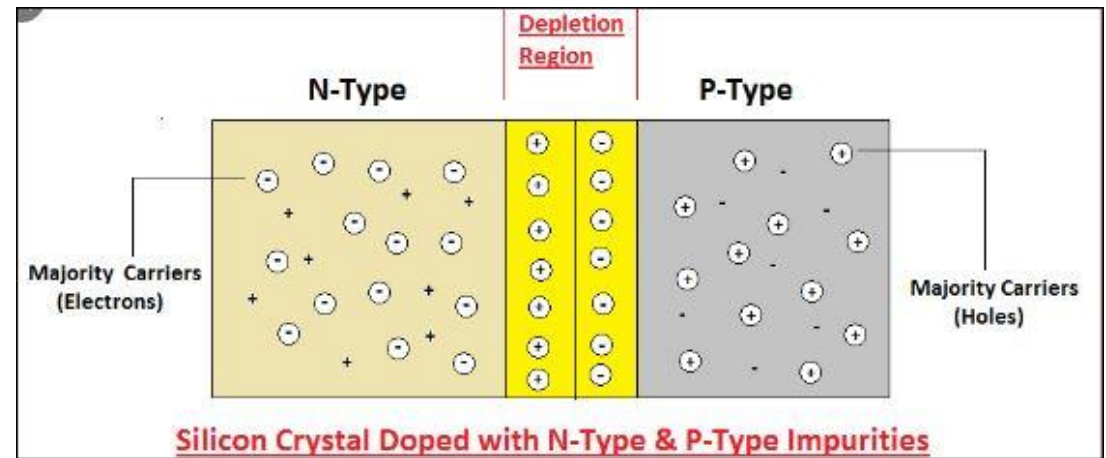

Potential Barrier:

- In depletion region many positive and negative charges on opposite side of the pn junction. Therefore Electric field is created inside the depletion region.
- Potential thus produced are called ..potential barrier. The amount of energy required to produce full conduction across the pn junction
- The electrons in the N region have to climb the potential hill in order to reach the P region
- Factors: type of semi-conductive material , the amount of doping and temperature.
- Barrier potential for silicon ---- 0.7 V and for Germanium ---0.3 V at 25°C.




Biasing

Bias is the application of a voltage across a pn junction.

- Forward biased PN junction
- Reverse biased PN junction

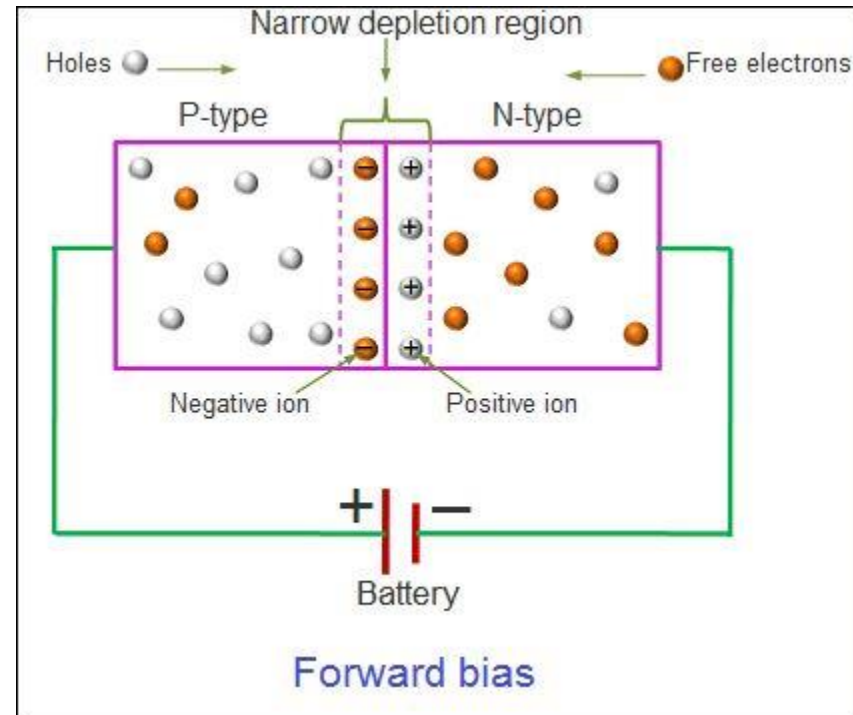- **Forward Bias:** is the condition that's allows current through pn junction,
- External voltage decreases width of potential barrier.
- **Requirements:**
- i) n-region connected to –ve terminal of the battery and p-region connected to +ve terminal of the battery.
- ii) Bias voltage must be greater than the barrier potential.




Reverse Bias:

pn junction blocks current in reverse bias
External voltage increases the built-in potential barrier.

p-region connected to +ve terminal of the battery
and n- region connected to -ve terminal of the battery.

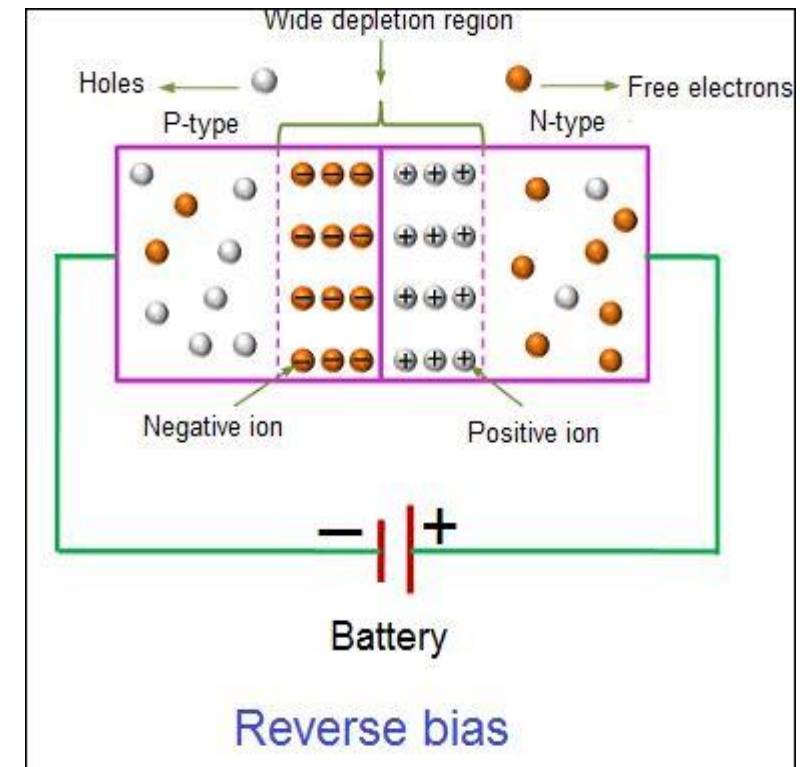Depletion region is wider in reverse biasing.



Bipolar Junction Transistors


- The transistor is a three-layer semiconductor device consisting of either two n- and one p- type layers of material or two p- and one n-type layers of material.
- The former is called an npn transistor, while the latter is called a pnp transistor
- So, there are two types of BJT
 - i) pnp transistor
 - ii) npn transistor



Bipolar Junction Transistors

In each transistor following points to be noted

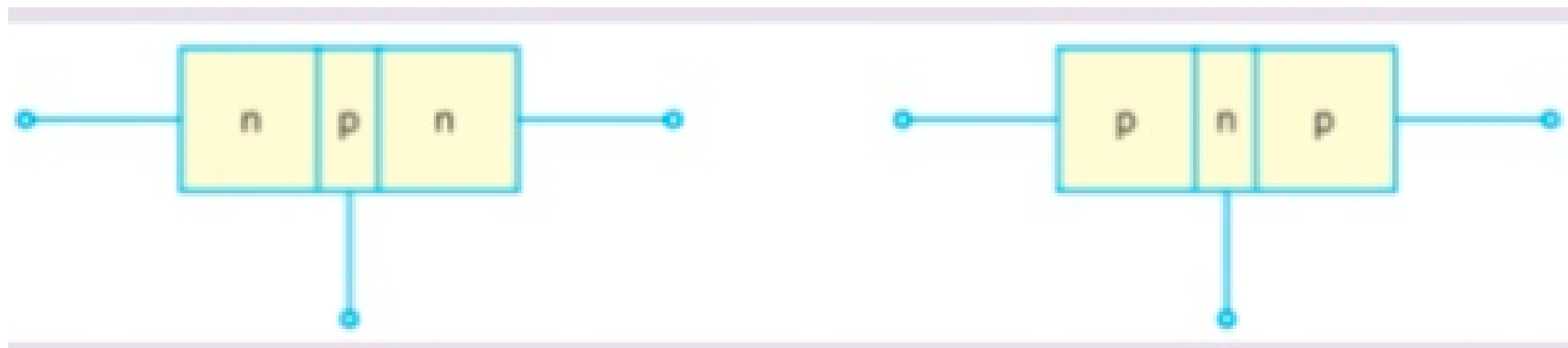- i) There are two junction, so transistor can be considered as two diode connected back to back.
- ii) There are three terminals.
- iii) The middle section is thin than other.



Some important factors to be remembered

- Emitter is heavily doped so it can inject large amount of carriers into the base.
- Base is lightly doped so it can pass most of the carrier to the collector.
- Collector is moderately doped.
- The junction between emitter and base is called emitter-base junction(emitter diode)
- The junction between base and collector is called collector-base junction(collector diode).
- The emitter diode is always forward biased and collector diode is reverse biased.



Naming of Transistor Terminals

- Transistor has three section of doped semiconductor.
- The section one side is called “emitter” and the opposite side is called “collector”. The middle section is called “base”.

Transistor symbol


Emitter:

- The section of one side that supplies carriers is called emitter.
- Emitter is always forward biased w.r.t base so it can supply carrier.
- For “npn transistor” emitter supply holes to its junction. For “pnp transistor” emitter supply electrons to its junction.

Collector:


- The section on the other side that collects carrier is called collector.
- The collector is always reversed biased wr to base.
- For “npn transistor” collector receives holes to its junction. For “pnp transistor” collector receives electrons to its junction.

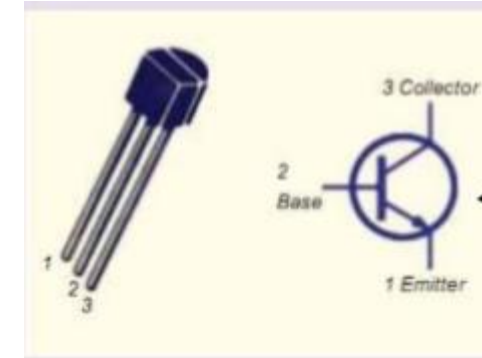Base: The middle section which forms two pn junction between emitter and collector is called Base.



Transistor Operation

- Working of npn transistor: Forward bias is applied to emitter- base junction and reverse bias is applied to collector- base junction. The forward bias in the emitter-base junction causes electrons to move toward base. This constitute emitter current, I_E
- As this electrons flow toward p-type base, they try to recombine with holes. As base is lightly doped only few electrons recombine with holes within the base. These recombined electrons constitute small base current I_B . The remainder electrons crosses base and constitute collector current I_C .
- $I_E = I_C + I_B$

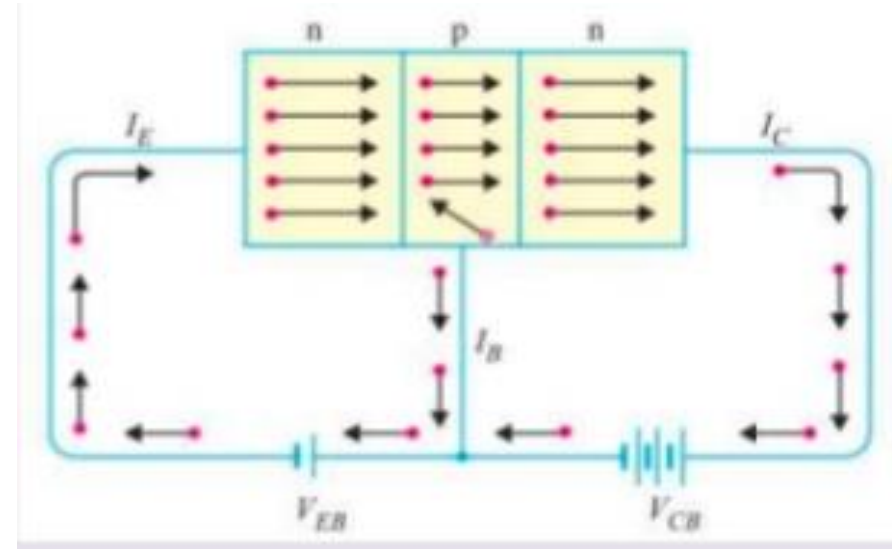

transistor Connection

Transistor can be connected in a circuit in following three ways

- 1) Common Base
- 2) Common Emitter
- 3) Common Collector

Common emitter configuration

$$I_E = I_C + I_B$$
$$\beta_{DC} = \frac{I_C}{I_B}, \alpha_{DC} = \frac{I_C}{I_E}$$
$$V_{in} = I_B R_1 + V_{BE}$$
$$V_{CC} = I_C R_2 + V_{CE}$$

Figure 1

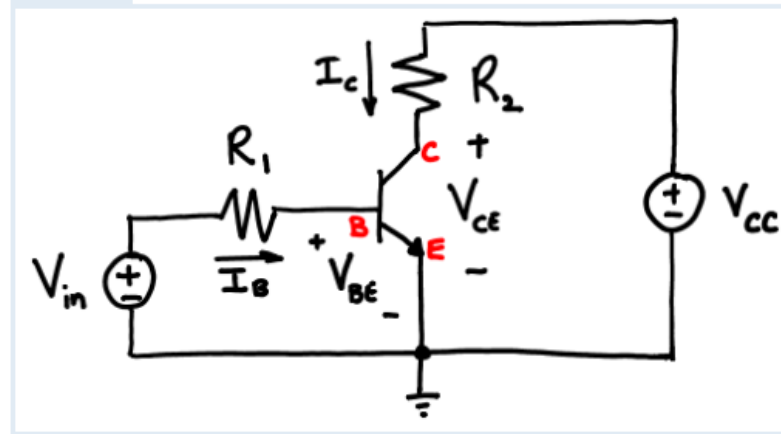



Fig. 1: Common emitter circuit. The emitter of the BJT is wired directly to ground. The input voltage source V_{in} is connected through resistor R_1 to the base. A constant voltage source V_{CC} is connected through resistor R_2 to the collector.



Problem

Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit of Figure 4–8. The transistor has a $\beta_{DC} = 150$.

► **FIGURE 4–8**

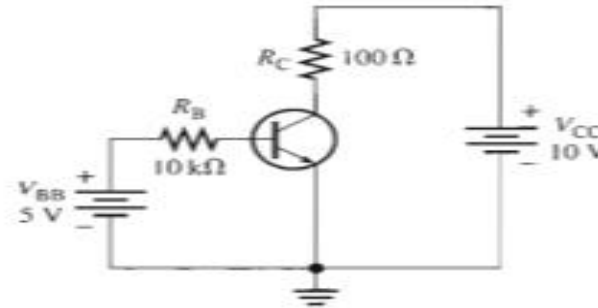

Solution From Equation 4–3, $V_{BE} \cong 0.7 \text{ V}$. Calculate the base, collector, and emitter currents as follows:

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 \text{ V} - 0.7 \text{ V}}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$$I_C = \beta_{DC} I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$$

$$I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu\text{A} = 64.9 \text{ mA}$$

Solve for V_{CE} and V_{CB} .

$$V_{CE} = V_{CC} - I_C R_C = 10 \text{ V} - (64.5 \text{ mA})(100 \Omega) = 10 \text{ V} - 6.45 \text{ V} = 3.55 \text{ V}$$


$$V_{CB} = V_{CE} - V_{BE} = 3.55 \text{ V} - 0.7 \text{ V} = 2.85 \text{ V}$$

Since the collector is at a higher voltage than the base, the collector-base junction is reverse-biased.



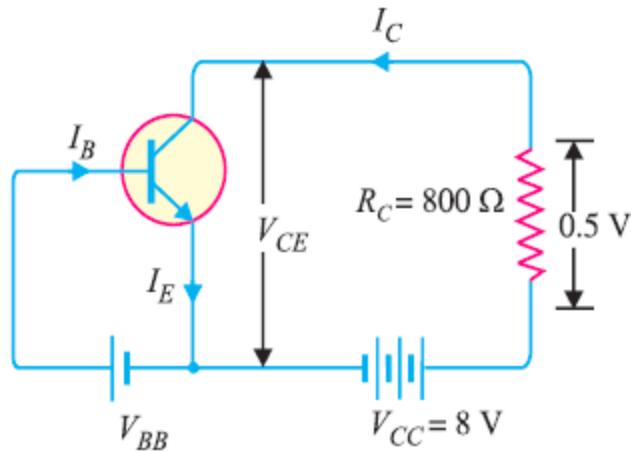problem

A transistor is connected in common emitter configuration in which collector supply is 8 V and the voltage drop across resistance R_C connected in the collector circuit is 0.5 V. The value of $R_C = 800 \Omega$. If $\alpha = 0.96$, determine : (i) collector-emitter voltage (ii) base current⁺



Collector-emitter voltage, (i)

$$V_{CE} = V_{CC} - 0.5 = 8 - 0.5 = 7.5 \text{ V}$$

(ii)

The voltage drop across $R_C (= 800 \Omega)$ is 0.5 V.

$$I_C = \frac{0.5 \text{ V}}{800 \Omega} = \frac{5}{8} \text{ mA} = 0.625 \text{ mA}$$

$$\text{Now } \beta = \frac{\alpha}{1 - \alpha} = \frac{0.96}{1 - 0.96} = 24$$

$$\therefore \text{ Base current, } I_B = \frac{I_C}{\beta} = \frac{0.625}{24} = 0.026 \text{ mA}$$

